

CSE - 306

Computer Architecture Sessional

4-bit ALU Design

Group - 02

Group members -

1905033

1905049

1905053

1905055

1905056

Introduction:

Arithmetic Logic Unit, which is known as 'ALU', is the part of a computer that performs all arithmetic computations, such as addition, multiplication and all comparison operations.

The arithmetic logic unit (ALU) represents the fundamental building block of the CPU (Central Processing Unit) of a computer. Examples of logic operations are NOT, AND, OR which are done by ALU. The arithmetic logic unit has two 4-bit input and three selection variables.

The selection bits enable different types of operation. $2^3 = 8$ operations are possible in our experiment. using the 4-bit inputs. In order to handle 4-bit inputs, 4-bit full adder (74LS83) is used.

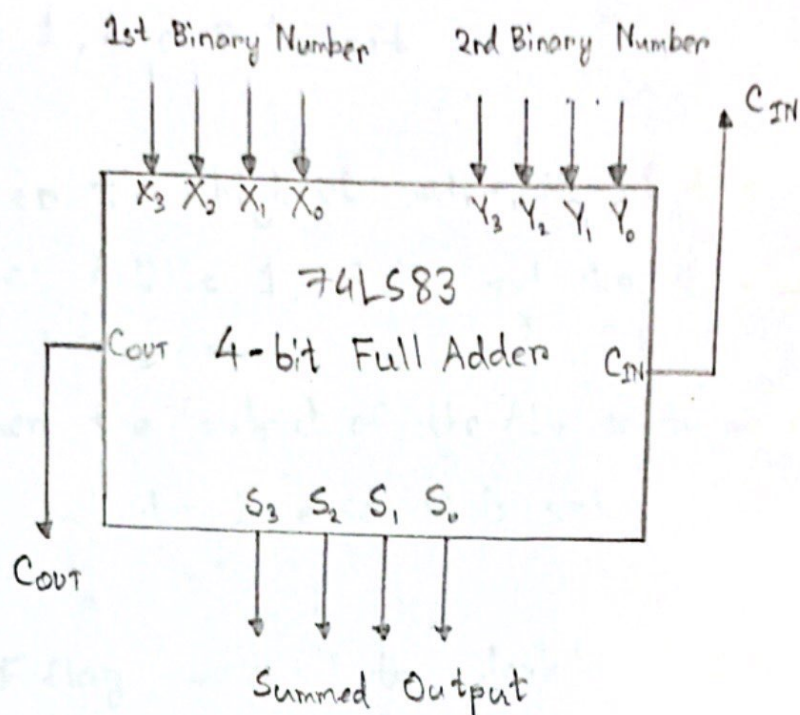


Fig: A 4-bit Full Adder

Different types of status arise while implementing arithmetic logic unit which are carry (C), sign (S), overflow (OV) and zero (Z). Different values appear in them in different operations of arithmetic logic unit.

CF: when the output carry of the 'ALU' becomes 1, CF is set to 1, else 0 is set.

OF: If the XOR of carries C_4 and C_8 is, V is set to 1, else 0 is set.

SF: When the highest order bit of the output of the ALU is 1, S is set to 1 else 0 is set.

ZF: When the output of the ALU contains all 0's, Z is set to 1 else 0 is set.

For OF flag, we need to calculate $C_3 \oplus C_4$ but we can't get directly C_3 from adder. So the value of OF is calculated in the following way,

$$\begin{array}{l|l} V = C_3 \oplus C_4 & C_3 = X_3 \oplus Y_3 \oplus S_3 \\ \Rightarrow V = (X_3 \oplus Y_3 \oplus S_3) \oplus C_4 & \end{array}$$

Here,

X and Y are the 4-bits inputs provided to the adder and S_3 is the MSB of summed output.

Problem Specification:

Design a 4-bit ALU with three selection bits

$cs_2(s)$, $cs_1(s)$, $cs_0(s)$ for performing the following operations,

C_{IN}			Operation	Output
s_2	s_1	s_0		
0	0	0	Transfer A	$F = A$
0	0	1	AND	$F = A \& B$
0	1	X	ADD	$F = A + B$
1	0	0	ADD with carry	$F = A + B + 1$
1	0	1	Complement A	$F = A'$
1	1	X	Decrement A	$F = A - 1$

Truth Table:

CS_2	CS_1	CS_0	X_i	Y_i	C_{in}	Output (F)
0	0	0	A_i	0	0	$F = A$
0	0	1	$A_i \oplus B_i$	0	0	$F = A \oplus B$
0	1	X	A_i	B_i	0	$F = A + B$
1	0	0	A_i	B_i	1	$F = A + B + 1$
1	0	1	\bar{A}_i	0	0	$F = A'$
1	1	X	A_i	1	0	$F = A - 1$

All 1's

Equations:

$$X_i = \bar{S}_0 A_i + S_1 A_i + \bar{S}_2 A_i B_i + S_2 \bar{S}_1 S_0 \bar{A}_i$$

$$Y_i = S_1 B_i + S_2 S_1 + S_2 \bar{S}_0 B_i$$

$$C_{in} = S_2 \bar{S}_1 \bar{S}_0$$

A_i	\bar{A}_i	$A_i \& B_i$	t_1	t_0
1	0	0	0	0
0	1	0	0	1
0	0	1	1	0

Truth table for 4x1 MUX selection bit of X_i

$$t_0 = \bar{A}_i \quad (\text{Decoder output } Y_5)$$

$$t_1 = A_i \& B_i \quad (\text{Decoder output } Y_1)$$

B_i	0	1	t_1	t_0
1	0	0	0	0
0	1	0	0	1
0	0	1	1	0

Truth table for 4x1 MUX selection bit of Y_i

$$t_1 = \text{OR of decoder output lines that give 1}$$

$$t_0 = \text{OR of decoder output lines that give 0}$$

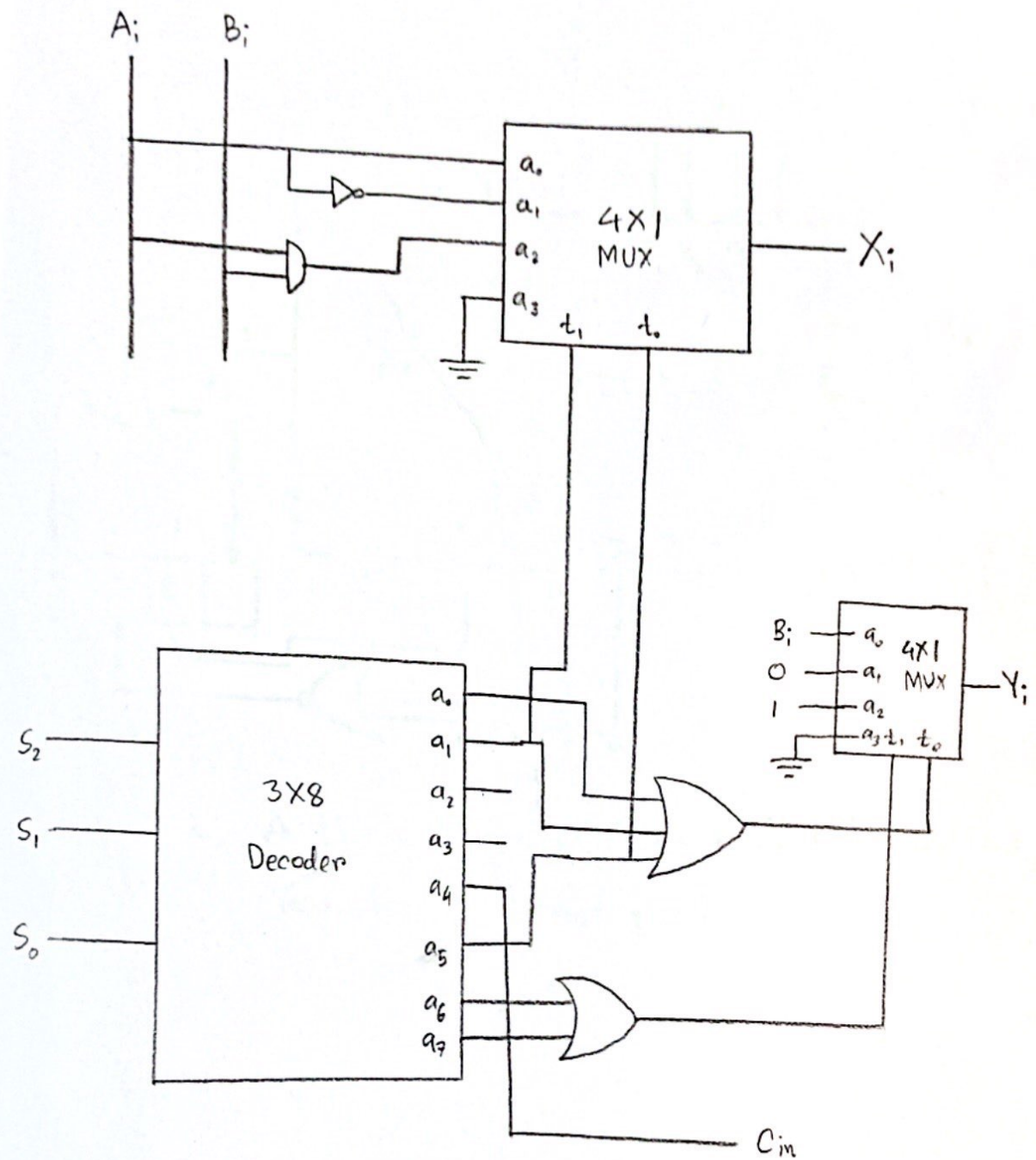


Fig 3: A block diagram to produce inputs of 4 bit adder.

 


Fig 2: A block diagram of an ALU with status registers. (External View)

Required ICs :

Name	Count
74238	1
74153	4
7404	1
7408	1
7432	2
7483	1
7486	1

Simulator: Logisim